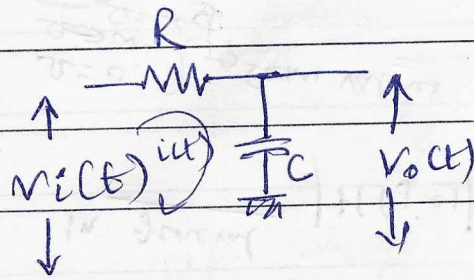


## RC filter



KVL:  $V_i(t) = iR + V_o(t) \rightarrow (1)$

Wkt:  $V_o(t) = V_c(t) = \frac{1}{C} \int i(t) dt$

DIFF. OBS.  $\frac{dV_o(t)}{dt} = \frac{1}{C} i(t)$

$i(t) = C \frac{dV_o(t)}{dt} \rightarrow (2)$

(2) in (1)

$$V_i(t) = RC \frac{dV_o(t)}{dt} + V_o(t)$$

In std form  $x(t) = RC y' + y(t)$




Ramaiah University of Applied Sciences

$$\text{LT} \Rightarrow V_i(s) = RCs V_o(s) + V_o(s)$$

$$\text{TF} \Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{1}{RCs + 1}$$

$$H(s) = \frac{1/RC}{s + 1/RC} \quad f_c = \frac{1}{2\pi RC}$$
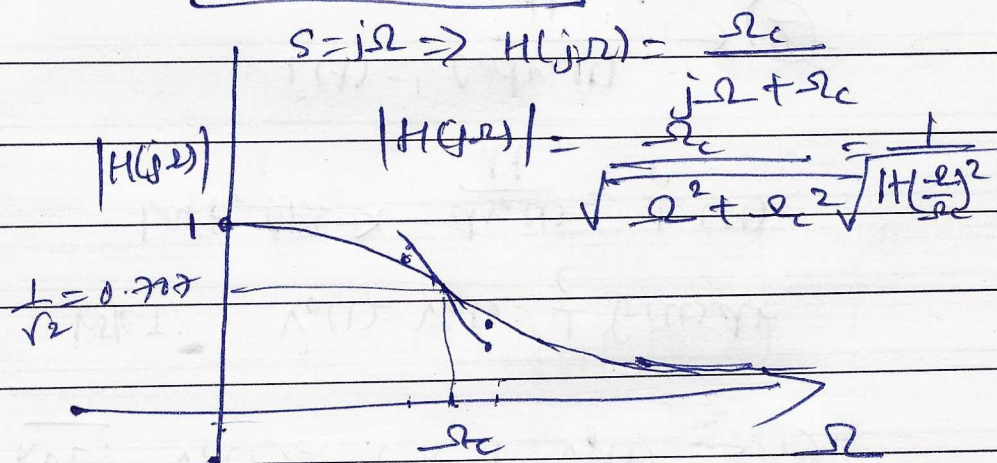
$$\boxed{H(s) = \frac{\omega_c}{s + \omega_c}} \quad \text{--- (3) ---} \quad \begin{aligned} 2\pi f_c &= \frac{1}{RC} \\ \omega_c &= \frac{1}{RC} \end{aligned}$$



In general  $|H(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^{2N}}}$

$\omega = 0$   
 $\omega \rightarrow \infty$   
 $\omega = \omega_c$  } Same values

$$\omega = \omega_c$$






$$1.21 \times 1.21$$

$$@ \Omega_c + 0.1 \Omega_c$$


$$|H(j\Omega)| = \frac{1}{\sqrt{1 + \left(\frac{\Omega_c + 0.1 \Omega_c}{\Omega_c}\right)^2}} = \frac{1}{\sqrt{1 + 1.1^2}} = \frac{1}{\sqrt{2.21}} = 0.67$$

$\Omega$	$\Omega_c$	$\Omega_c + 0.1 \Omega_c$	$\Omega_c$	$\Omega_c + 0.1 \Omega_c$	$\Omega \rightarrow \infty$
$N=1$	1	0.74	0.707	0.67	0
$N=2$	1	0.77	0.707	0.68	0
$N=3$	1	0.808	0.707	0.60	0

$$|H(j\Omega)| = \frac{1}{\sqrt{1 + \left(\frac{\Omega}{\Omega_c}\right)^2}} = \frac{1}{\sqrt{1 + (\Omega)^2}}$$

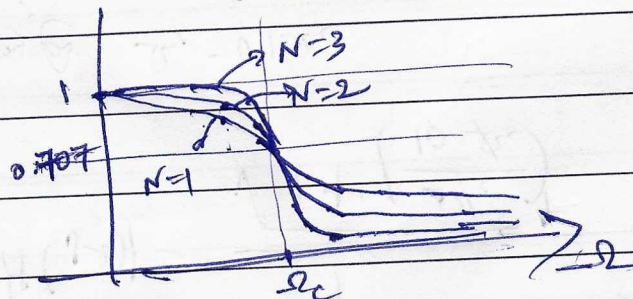

Ramaiah University of Applied Sciences

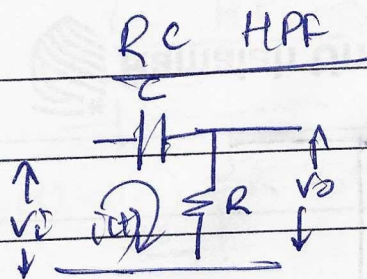

KVL

$$V_i(t) = V_C(t) + V_o$$

WET  $V_o(t) = i(t)R$

$$i(t) = \frac{V_o(t)}{R}$$

$$V_C(t) = V_i(t) - V_o(t)$$

$$V_i(t) = \frac{1}{C} \int i(t) dt + V_o(t)$$

$$i(t) = C \frac{dV_C}{dt} = C \frac{d(V_i - V_o)}{dt}$$

$$V_i(t) = V_o(t) + \frac{1}{C} \int i(t) dt$$

$$V_i(t) = V_o(t) + \frac{1}{C} \int \frac{V_o(t)}{R} dt$$

$$V_i(t) = V_o(t) + \frac{1}{RC} \int V_o(t) dt$$

Diff obs  $\frac{dV_i(t)}{dt} = \frac{dV_o(t)}{dt} + \frac{V_o(t)}{RC}$

$$V_o(t) = RC \left[ \frac{dV_i(t)}{dt} - \frac{dV_o(t)}{dt} \right]$$

$$V_o(s) = RCS V_i(s) - RCS V_o(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{RCS}{1 + RCS}$$



Ramaiah University of Applied Sciences




$$H(s) = \frac{s}{s + \frac{1}{RC}} = \frac{s}{s + \omega_c}$$

$$H(j\omega) = H(s)|_{s=j\omega} = \frac{j\omega}{j\omega + \omega_c}$$

$$|H(j\omega)| = \frac{\sqrt{\omega^2}}{\sqrt{\omega^2 + \omega_c^2}} = \frac{\omega}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^{2n}}}$$

$\omega$	$\omega=0$	$\omega=0.9\omega_c$	$\omega=\omega_c$	$\omega=1.1\omega_c$	$\omega \rightarrow \infty$
$n=1$	0		0.707		1
$n=2$	0		0.707		1
$n=3$	0		0.707		1
$n=5$	?	?	?	?	?

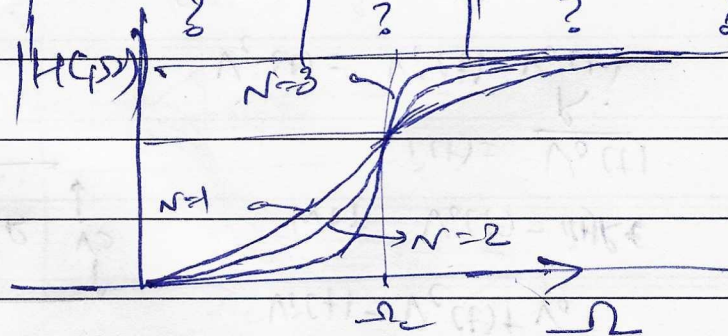

Ramaiah University of Applied Sciences